

# Outputs


Amber LED connector

## inputs

### Schematic

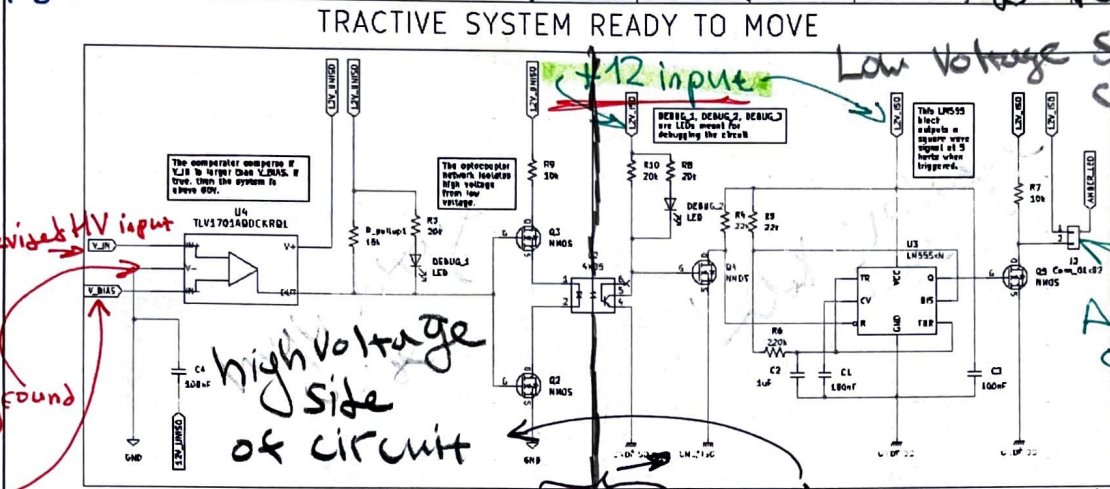
## Labeling inputs / outputs

can see circuit is fully separated into high voltage side and low voltage side as per regulations



Low Voltage Side of circuit

Amber LED output

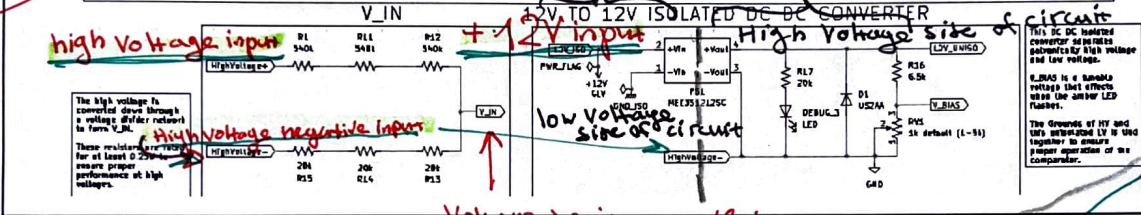


Voltage Divider Calculation  
When high is voltage

High Voltage Input

$$V_{out} = \left( \frac{R_2}{R_1 + R_2} \right) V_{in}$$

this circuit
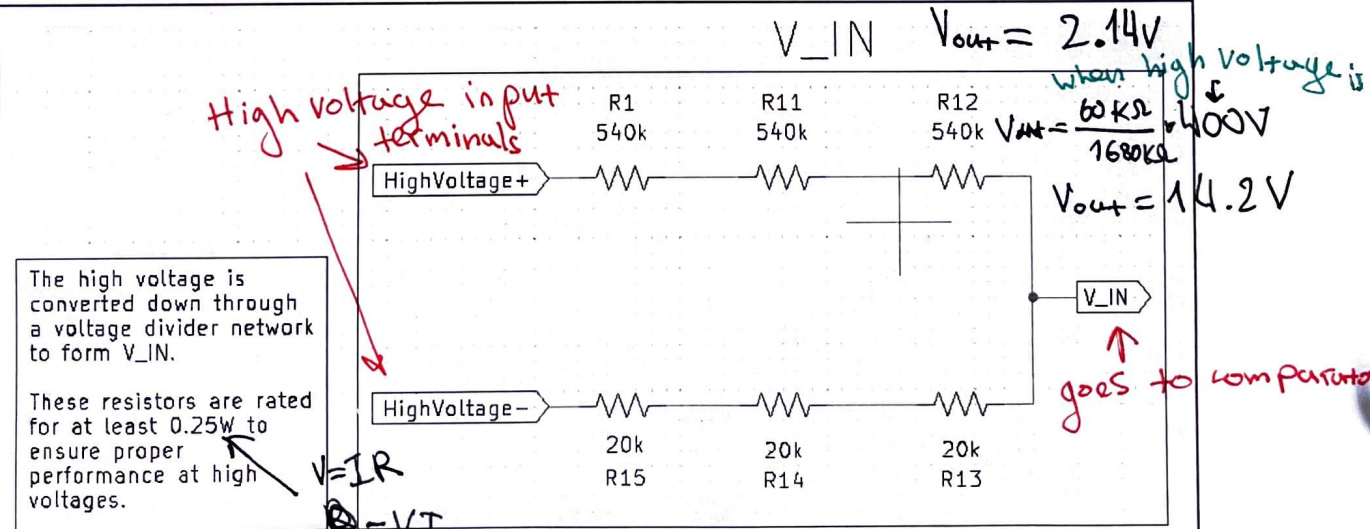
$$V_{out} = \frac{60K\Omega}{1680K\Omega} \cdot (60V)$$



The high voltage is converted down through a voltage divider network to form V\_IN.

These resistors are rated for at least 0.25W to ensure proper performance at high voltages.

$$V = IR$$

$$P = VI$$

$$0.25W = 400V \cdot I$$

This is a voltage divider network that converts high voltage (up to around 460V) to around

$R_{total} = 1680,000\Omega$

Max I through circuit is 0.625 mA at 400V

$V = IR$

$400 = I \cdot 1680,000\Omega$

at 400V  $I = 0.238 \text{ mA}$  at through this circuit which means 0.25W is more than enough




Electronically isolates two grounds  
input ground and output ground are not electronically connected

## 12V-12V Isolated DC-DC Converter

Converter will block short circuit currents from entering low voltage side  
thus there is short circuit on low voltage side high current from high voltage side will not pass

## 12V TO 12V ISOLATED DC DC CONVERTER

Regular 12V input

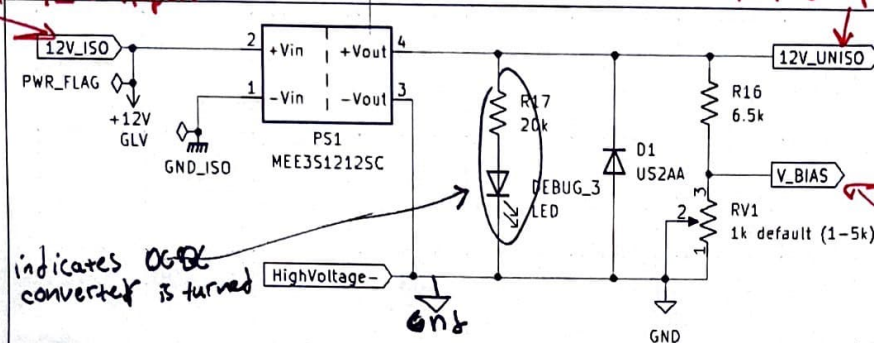

indicates DC-DC converter is turned on

This DC DC isolated converter separates galvanically high voltage and low voltage.

V\_BIAS is a tunable voltage that affects when the amber LED flashes.

The Grounds of HV and this unisolated LV is tied together to ensure proper operation of the comparator.

Vref for comparator to provide sufficient reference

A 12V to 12V Isolated DC-DC Converter ensures that high voltage and low voltage are sufficiently isolated. Make sure to choose one with a voltage isolation of over 500V.

The Zener diode D1 is used as an ESD protection diode. Make sure it triggers at 15V to prevent excessive voltage.

There is a potentiometer (from 1 to 5k) that will be used to vary the bias voltage.


(2.14V)

$$12V \cdot \frac{2k}{8.5k} = 2.8V$$

RV1 should be set to slightly below 2k

note that V\_Bias (Vref for comparator) has ground ~~from~~ shared from High Voltage side

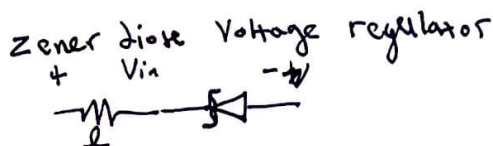Zener diode designed to conduct current in reverse direction at specific "Zener Voltage"  
Zener diodes are used in voltage regulation  
for low current tasks




zener diode will regulate voltage across it by sending excess voltage away if it is higher than zener voltage to be dropped by resistor in series

in this case zener diode pulls outputs to ground on high side 12V\_UNISO and V-Bias when Vout from converter exceeds zener voltage threshold preventing comparator from receiving measurements to compare

## Input Stage: Comparator

isolated 12V from low voltage side

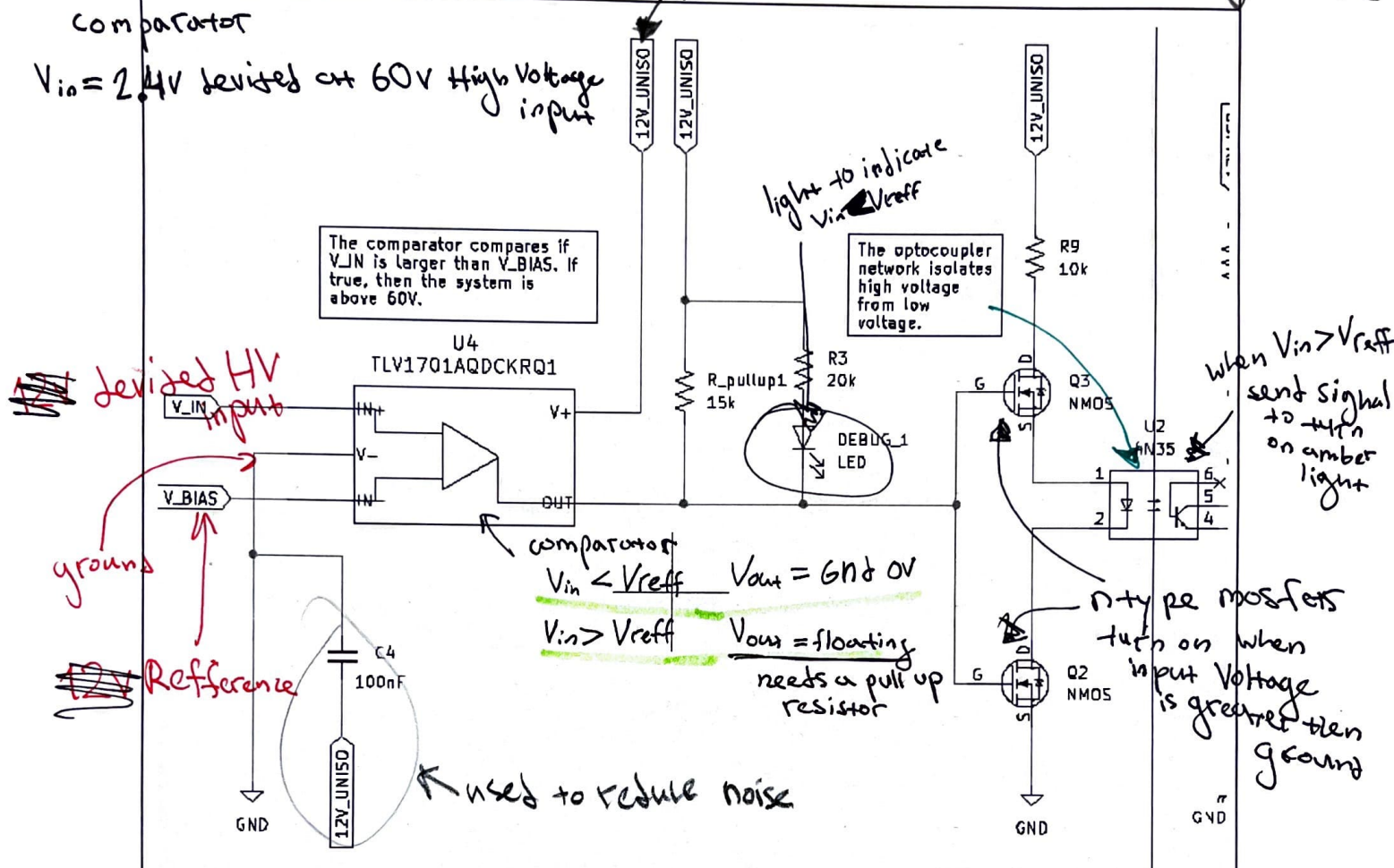

If  $V_{IN}$  is higher than  $V_{BIAS}$ , then it means that the high voltage is larger than 60 volts.

Thus, this comparator will produce a high signal and turn on NMOS Q3 and NMOS Q2, which will turn on the optocoupler.

This NMOS Q2 and Q3 network helps to isolate the optocoupler when HV is floating, off, and on.

Resistor values (10k, 15k, 20k) can all be set to 22k (or any other **larger value**) for convenience.

Both inputs  $V_{ref}$  and  $V_{in}$  (deviated high Volt input) have same ground  $\leftarrow$  thus op amp comparator can compare voltages correctly (need to share common ground)

highside ground



DEBUG\_1, DEBUG\_2, DEBUG\_3 are LEDs meant for debugging the circuit.

This LM555 block outputs a square wave signal at 5 hertz when triggered.

resistor in place is connected to the 12V ISO supply.

On when signal from optocoupler is low  
Off when signal from optocoupler is high

h type mosfet

On when signal from optocoupler is low  
Off when signal from optocoupler is high

control Reset pin on 555 timer  
When reset is pulled down low 555 timer is off  
thus when optocoupler signal is low reset pin on 555 timer is grounded by Q4

The 555 timer block produces a 5 Hz signal to trigger the AMBER LED.

Note that the AMBER LED is configured assuming the ground switching configuration.

Capacitor values must be EXACT to produce a 5 Hz signal.

output of 555 timer pulses Nmos which turns on/off amber by tying it down to ground

High signal  
means turn on  
amber light<sup>DS</sup>


controls Reset pin on 555 timer  
When Reset is pulled down low 555 timer is off  
When octopus signal is low reset pin on 555 timer is grounded by Q4 mosfet  
The 555 timer block produces a 5 Hz signal to trigger the AMBER LED.

Note that the AMBER LED is configured assuming the ground switching configuration.

Capacitor values must be EXACT to produce a 5 Hz signal.


# FSAE Notes

tractive system ready to move

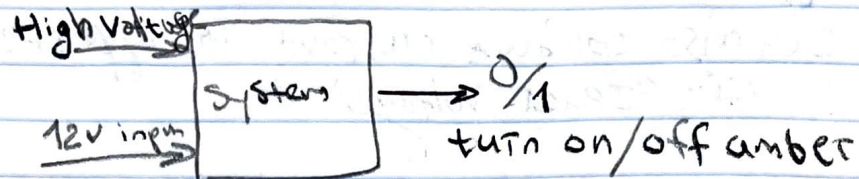


indicates weather high voltage is present with flashing amber Light

based on Voltage Op amp Comparator

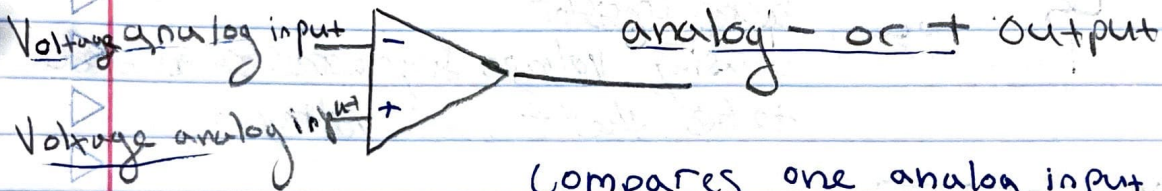

Compares one analog input voltage level with Voltage Reference

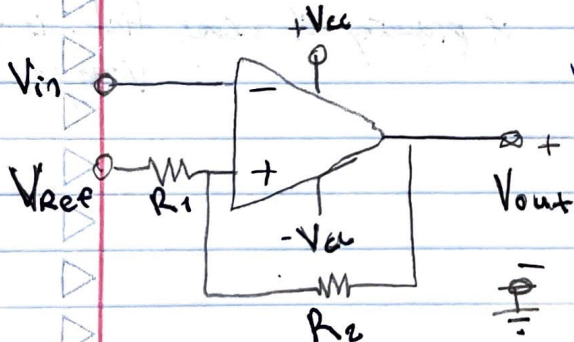↓  
produces output based on voltage comparison




Output (analog not digital)

if  $V_{in} > V_{REF}$  then  $V_{out} = +V_{CC}$

if  $V_{in} < V_{REF}$  then  $V_{out} = -V_{CC}$

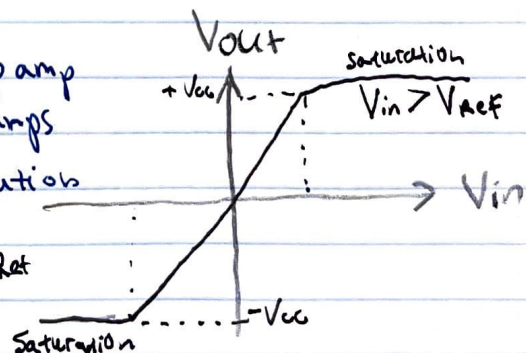as you can see from graph Opamp Voltage comparator is just op amps set up to easily reach saturation when seeing signal difference



Value on output is dependent on  $V_{CC}$  voltage



## zener diode

↳ acts like a regular diode




conducting current only in one way


↓  
can also conduct current in opposite direction at a specific "zener voltage"

↳ can be used as voltage regulator to maintain a stable voltage
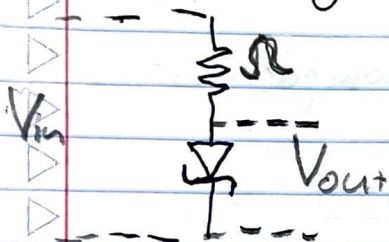
### Simple Voltage regulator using zener diode



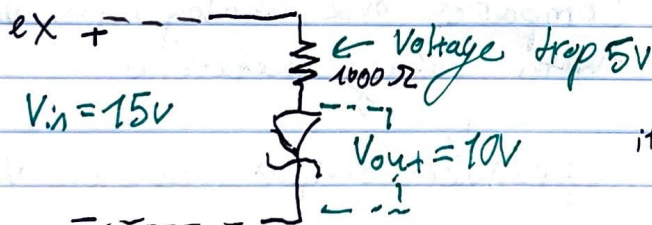regulates output voltage across zener diode by dumping excess voltage to voltage drop across resistor causing voltage drop across zener diode to be the "zener voltage"



if property of zener diode is zener voltage 10V